
Using the AD5206 digital potentiometer with AC signals

- The AD5206 behaves like six mechanical potentiometers.
- Each potentiometer has three terminals (A,B, and W), just like a mechanical.
- These potentiometers are (to the best of my knowledge) completely isolated—I did not observe any leakage between them.
- There are two power terminals on the chip: V_{SS} and V_{DD} .
- These terminals are subject to the constraints that

$$V_{SS} \leq 0 \leq V_{DD}$$

and

$$|V_{DD}| + |V_{SS}| \leq 5.5V$$

- The potentials of all three wiper terminals MUST be between V_{SS} and V_{DD} :

$$V_{SS} \leq \{A, B, W\} \leq V_{DD}$$

- If this condition is not met, the response is nonlinear, and signals are distorted.

Monopolar Mode

These potentiometers are usually used in (and most online resources assume) monopolar mode

- In this mode, $V_{SS} = 0V = \text{GND}$, and $V_{DD} = 5V$.
- This is very convenient, since the logic output of most microcontrollers (e.g. Arduino) is $5V$, so no step-down is needed.
- However, because of the voltage bounds mentioned above, this means we can't send zero-offset AC signals (like we're working with here) through the digipot
- We could add an offset using an opamp, but that makes scaling very difficult, and adds unnecessary noise.

Bipolar Mode

Instead, we can operate in bipolar mode, where $V_{SS} < 0$. Some considerations in this mode:

- The potential bounds still apply. If we power the digipot with $\pm 2.5V$, the signal must fall within those bounds as well. This should not be a problem, since our signal should be within the $\pm 1V$ envelope.
- The logic voltage must be within $0.3V$ of V_{DD} (or specifically, when $V_{DD} = 3V$, the logic must be between $2.6V$ and $3.3V$, as per the datasheet).
- Logic low is still ground.
- There are $3.3V$ logic Arduinos, which could directly drive the chip in this mode. I am looking to acquire one of these, to eliminate the three voltage dividers needed with a $5V$ arduino.

Communication

- We communicate with the potentiometer using SPI (serial peripheral interface).
- To set a resistance:
 - Drive the CS (chip select) pin low
 - Write the address as a single byte, MSB first. Because valid addresses are 0 – 5 (zero-indexed), the word will look like `0b00000101` (for address 5).
 - In Arduino, this can be done with `SPI.transfer(channel)`, where `channel` is in the range 0 – 5.
 - Then write the desired potentiometer value as a single byte, ranging from 0 (minimum resistance) to 255 (maximum resistance). In theory, the output resistance at step n will be

$$R_{\text{out}} = (n/255) \cdot 50 \text{ k}\Omega$$

Experimental response curves are detailed below.

- Drive the CS pin high.
- The code used on the Arduino is in the associated Github repository.

Odds and ends

- During testing, I used an external power supply tuned to $\pm 2.5V$. However, to simplify the circuit (the less wires running on and off the board, the better), I am using voltage dividers off the $\pm 15V$ opamp bus.
- Because of gaps in our resistor set, I was not able to power the chip at $\pm 2.5V$. Instead, it is powered at $-2V/+3V$. This should not present a problem, since it still gives us the $\pm 2V$ envelope, which should be sufficient.
- IMPORTANT!!! The AD5206 comes in three varieties—10 k Ω , 50 k Ω , and 100 k Ω . The 10 and 100 varieties DO NOT respond properly in bipolar mode. This was not documented anywhere, but only the 50 k Ω works for our purposes.
- The only possible explanation I was able to find is that the 50 k Ω is listed as RoHS compliant on DigiKey, while the others are not. The 50 k Ω could therefore be a newer make. This stymied me for about 5 days, since I was using a 100 k Ω .

Response curves

Potentiometer	Base resistance (Ω)	Response (Ω /tick)
Ideal	50 ¹	196.1
R1	30.3	202.6
R2	39.5	202.3
R3	39.9	202.1
R4	42.0	202.1
R5	10.9	202.6
R6	27.4	202.4

These resistors have a small (near-negligible) wiper resistance, and a slightly higher maximum resistance than advertised. The typical maximum resistance was about 51.5 k Ω . No statistically significant nonlinearity was observed.

¹ “Typical” wiper resistance from datasheet